

Übungsblatt - Widerstandsnetzwerk


Beispiel c)

$$U_B = 12 \text{ V}$$

$$R_1 = 120 \, \Omega$$

$$R_2 = 3,3 \text{ k}\Omega$$

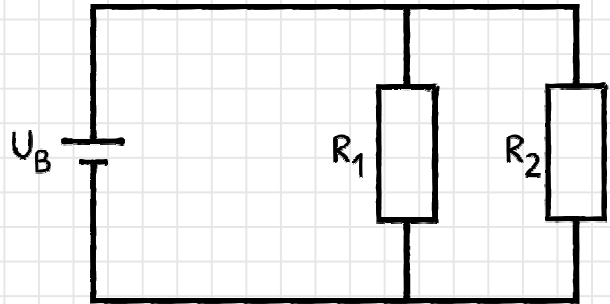gesucht: R_{ges} , U_{R1} , I_{R1} , U_{R2} , I_{R2} ,



gegeben:

$$U_B := 12 \text{ V}$$

$$R_1 := 120 \, \Omega$$

$$R_2 := 3,3 \text{ k}\Omega$$

Berechnung:

$$U_{R1} := U_B = 12 \text{ V}$$

$$U_{R2} := U_B = 12 \text{ V}$$

$$R_{\text{ges}} := \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = 115,7895 \, \Omega$$

$$I_{\text{ges}} := \frac{U_B}{R_{\text{ges}}} = 0,1036 \text{ A}$$

$$I_{\text{ges}} = 103,6364 \text{ mA}$$

$$I_{R1} := \frac{U_{R1}}{R_1} = 0,1 \text{ A}$$

$$I_{R1} = 100 \text{ mA}$$

$$I_{R2} := \frac{U_{R2}}{R_2} = 0,0036 \text{ A}$$

$$I_{R2} = 3,6364 \text{ mA}$$